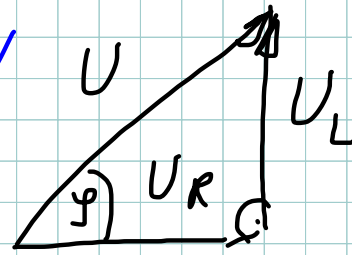


$$103/3 \quad \varphi = 60^\circ \quad U_R = 120V$$



$$U = \frac{U_R}{\cos \varphi} = \frac{120}{\cos 60} = 240V$$

$$U_L = \sqrt{U^2 - U_R^2} = \sqrt{240^2 - 120^2} = 207,8V$$

$$\begin{aligned} \tan \varphi = \frac{U_L}{U_R} &\Rightarrow U_L = U_R \cdot \tan \varphi = \\ &= 120 \cdot \tan 60 = \\ &= 207,8V \end{aligned}$$


103/4

$$R = 26 \Omega$$

$$U = 230 \text{ V}$$

$$f = 50 \text{ Hz}$$

$$I = 6,8 \text{ A}$$

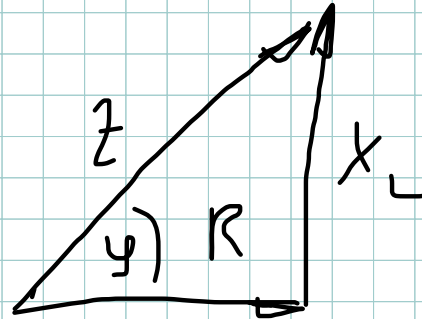

$$Z = \frac{U}{I} = \frac{230}{6,8} = 33,8 \Omega$$

$$X_L = \sqrt{Z^2 - R^2} = \sqrt{33,8^2 - 26^2} = 21,6 \Omega$$

$$L = \frac{X_L}{2 \pi f} = \frac{21,6}{2 \cdot \pi \cdot 50} = 68,9 \text{ mH}$$

$$U_R = I \cdot R = 6,8 \cdot 26 = 176,8 \text{ V}$$

$$U_L = I \cdot X_L = 6,8 \cdot 21,6 = 146,9 \text{ V}$$

103/5


$$U = 230 \text{ V}$$

$$f = 50 \text{ Hz}$$

$$\cos \varphi = 0,6$$

$$I = 0,18 \text{ A}$$
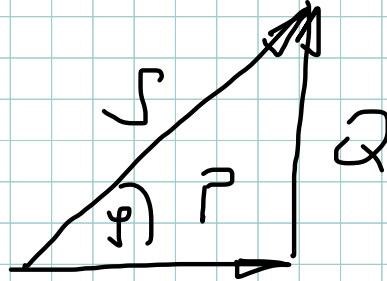
$$S = U \cdot I = 230 \cdot 0,18 = 41,4 \text{ VA}$$



$$P = S \cdot \cos \varphi = 41,4 \cdot 0,6 = 24,84 \text{ W}$$


$$Q = \sqrt{S^2 - P^2} = \sqrt{41,4^2 - 24,84^2} = 33,1 \text{ Var}$$

103/10

$$U = 230 \text{ V}$$

$$I = 0,43 \text{ A}$$

$$\cos \varphi = 0,45$$

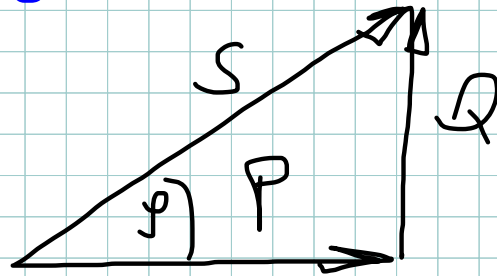


$$S = U \cdot I = 230 \cdot 0,43 = 98,9 \text{ VA}$$

$$P = S \cdot \cos \varphi = 98,9 \cdot 0,45 = 44,5 \text{ W}$$

$$Q = \sqrt{S^2 - P^2} = \sqrt{98,9^2 - 44,5^2} = 88,3 \text{ Var}$$

103/13

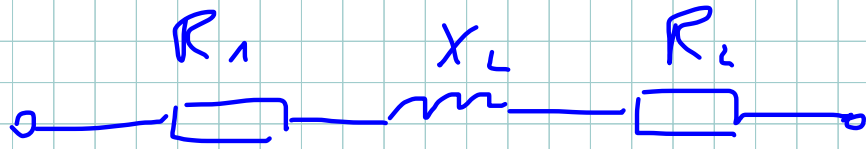


$$U = 230 \text{ V}$$

$$f = 50 \text{ Hz}$$

$$R_1 = 30 \Omega$$

$$P_2 = 25 \text{ W}$$

$$U_2 = 100 \text{ V}$$

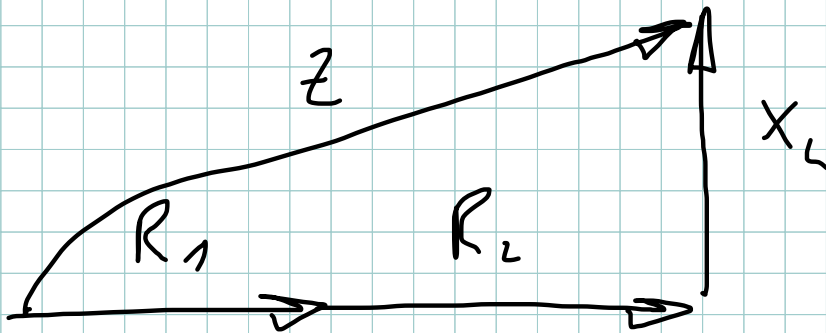

$$I = \frac{P_2}{U_2} = \frac{25}{100} = 0,25 \text{ A}$$

$$R_2 = \frac{U_2}{I} = \frac{100}{0,25} = 400 \Omega$$

$$Z = \frac{U}{I} = \frac{230}{0,25} = 920 \Omega$$

$$R_g = R_1 + R_2 = 30 + 400 = 430 \Omega$$

$$X_L = \sqrt{Z^2 - R^2} = \sqrt{920^2 - 430^2} = 813,3 \Omega$$

$$L = \frac{X_L}{2\pi f} = \frac{813,3}{2 \cdot \pi \cdot 50} = 2,59 \text{ H}$$

$$P = I^2 \cdot R = 0,25^2 \cdot 430 = 26,9 \text{ W}$$

$$S = U \cdot I = 230 \cdot 0,25 = 57,5 \text{ VA}$$

$$Q = \sqrt{S^2 - P^2} = \sqrt{57,5^2 - 26,9^2} = 50,8 \text{ Var}$$

Zeigerdiagramm:

$$I = 0,25 \text{ A} \rightarrow 5 \text{ cm}$$

$$U_{R1} = 7,5 \text{ V} \rightarrow 3,75 \text{ mm}$$

$$U_{R2} = 100 \text{ V} \rightarrow 5 \text{ cm} \quad 20 \text{ V} \hat{=} 1 \text{ cm}$$

$$U_L = 203 \text{ V} \rightarrow 10 \text{ cm} \quad 0,25 \text{ A} \hat{=} 5 \text{ cm}$$

$$U = 230 \text{ V} \rightarrow 11,5 \text{ cm}$$