

$$1.4 \quad R = 40 \Omega$$

$$U = 230V$$

$$I = ?$$

$$I = \frac{U}{R} = \frac{230}{40} =$$

$$= 5,75 A$$

$$1.5 \quad U = 230V$$

$$I = 273 \text{ mA}$$

$$R = ?$$

$$R = \frac{U}{I} = \frac{230}{273 \text{ m}} =$$

$$= 842,5 \Omega$$

$$1.6 \quad I = 6 \text{ A}$$

$$R = 60 \text{ m}\Omega$$

$$U = ?$$

$$U = \underline{I} \cdot R = 6 \cdot 60 \text{ m} = \\ = 360 \text{ mV} = 0,36 \text{ V}$$

$$1.7 \quad U = 230 \text{ V}$$

$$R = 24,2 \Omega$$

$$I = ?$$

$$I = \frac{U}{R} = \frac{230}{24,2} = 9,5 \text{ A}$$

$$1.8 \quad R = 1000 \Omega$$

$$U = 24 \text{ V}$$

$$I = ?$$

$$I = \frac{U}{R} = \frac{24}{1000} = 24 \text{ mA} \\ = 0,024 \text{ A}$$

$$1.9 \quad U = 6V \quad I = 0,3A$$

$$R = \frac{U}{I} = \frac{6}{0,3} = 20 \Omega$$

$$1.10 \quad R = 1,8 k\Omega \quad I = 11mA$$

$$U = I \cdot R = 11mA \cdot 1,8 k\Omega \\ = 19,8V$$

$$1.11 \quad R = 2,2 k\Omega \quad U = 9,6V$$

$$I = \frac{U}{R} = \frac{9,6}{2,2 k} = 4,36mA$$

$$1.12 \quad I = 3mA \quad R = 1k\Omega$$

$$U = I \cdot R = 3mA \cdot 1k\Omega \\ = 3V$$