
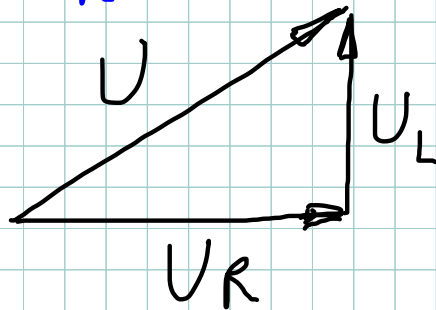


$$18.1 \quad U_R = 30V \quad U_L = 40V$$

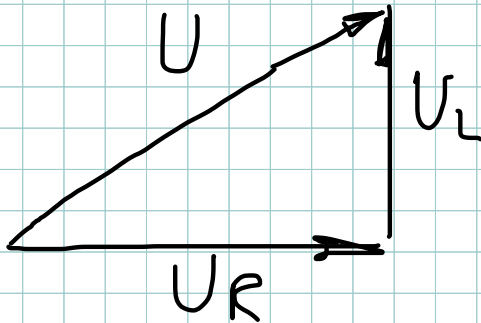


$$U = \sqrt{U_R^2 + U_L^2} = \sqrt{30^2 + 40^2} = 50V$$

$$18.2 \quad U = 230V \quad U_L = 185V$$



$$U_R = \sqrt{U^2 - U_L^2} = \sqrt{230^2 - 185^2} = 136,7V$$

$$18.3 \quad U = 42V \quad U_R = 36V$$

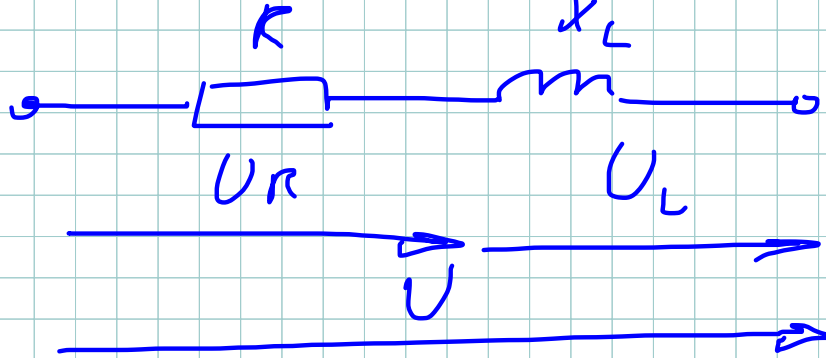

$$U_L = \sqrt{U^2 - U_R^2} = \sqrt{42^2 - 36^2} = 21,6V$$

$$18.4 \quad R = 250\Omega \quad L = 0,8H$$


$$f = 50Hz \quad U = 230V$$

$$X_L = 2\pi fL = 2 \cdot \pi \cdot 50 \cdot 0,8 = 251,3\Omega$$

$$Z = \sqrt{R^2 + X_L^2} = \sqrt{250^2 + 251,3^2} = 354,5\Omega$$

$$18.5 \quad f = 3 \text{ kHz} \quad R = 3,3 \text{ k}\Omega$$

$$Z = 3,75 \text{ k}\Omega$$

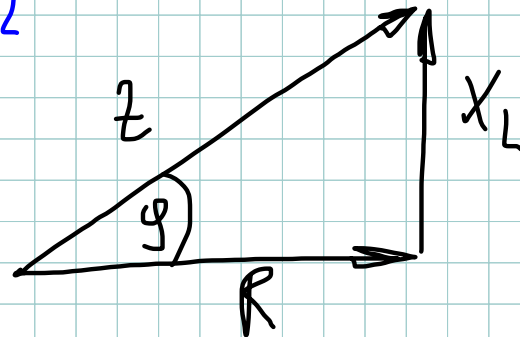

$$X_L = \sqrt{Z^2 - R^2} = \sqrt{3,75 \text{ k}^2 - 3,3 \text{ k}^2} = 1,78 \text{ k}\Omega$$

$$L = \frac{X_L}{2\pi f} = \frac{1,78 \text{ k}}{2 \cdot \pi \cdot 3 \text{ k}} = 94,5 \text{ mH}$$

$$18.6 \quad f = 50 \text{ Hz} \quad X_L = 230 \Omega$$

$$Z = 300 \Omega$$

$$R = \sqrt{Z^2 - X_L^2} = \sqrt{300^2 - 230^2} = 193 \Omega$$

$$18.7 \quad L = 200 \text{ mH} \quad f = 3,4 \text{ kHz}$$

$$Z = 4,3 \text{ k}\Omega$$

$$X_L = 2\pi fL = 2 \cdot \pi \cdot 3,4 \text{ k} \cdot 200 \text{ m} =$$
$$= 4,27 \text{ k}\Omega$$

$$R = \sqrt{Z^2 - X_L^2} = \sqrt{4,3 \text{ k}^2 - 4,27 \text{ k}^2} =$$
$$= 485 \Omega$$

$$\text{Markiert: } 500 \Omega \hat{=} 1 \text{ cm}$$

$$18.8 \quad f = 50 \text{ Hz}$$

$$U = 6,3 \text{ V} \quad I = 23 \text{ mA}$$

$$R = 36 \, \Omega$$


$$Z = \frac{U}{I} = \frac{6,3}{23 \text{ mA}} = 274 \, \Omega$$

$$X_L = \sqrt{Z^2 - R^2} = \sqrt{274^2 - 36^2} = 272 \, \Omega$$

$$18.9 \quad U = 60 \text{ V} \quad \cos \varphi = 0,28$$

$$\varphi = \arccos(0,28) = 73^\circ$$

$$\cos \varphi = \frac{U_R}{U}$$

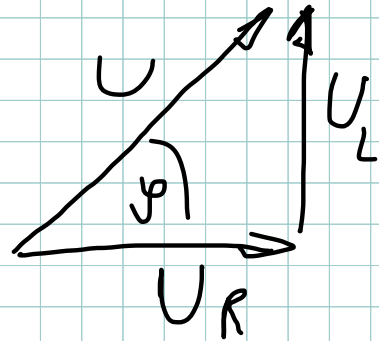

$$U_R = U \cdot \cos \varphi = 60 \cdot 0,28 = 16,8 \text{ V}$$

$$U_L = \sqrt{U^2 - U_R^2} = \sqrt{60^2 - 16,8^2} = 57,6 \text{ V}$$


Maßstab: $10 \text{ V} \hat{=} 1 \text{ cm}$

$$18.10 \quad U_R = 160V \quad \cos \varphi = 0,45$$

$$\cos \varphi = \frac{U_R}{U}$$


$$U = \frac{U_R}{\cos \varphi} = \frac{160}{0,45} = 356V$$
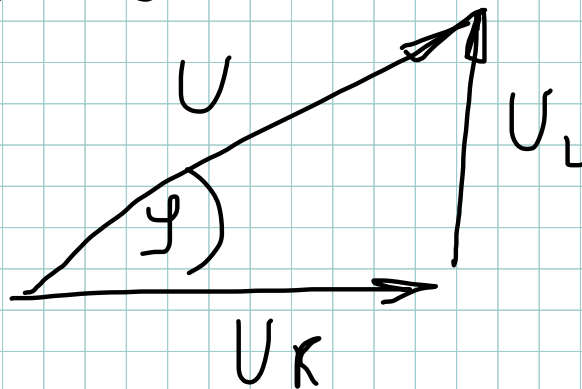
$$U_L = \sqrt{U^2 - U_R^2} = \sqrt{356^2 - 160^2} = 318V$$



$$18.11 \quad R = 32 \, \Omega \quad f = 50 \text{ Hz}$$

$$\cos \varphi = 0,12$$

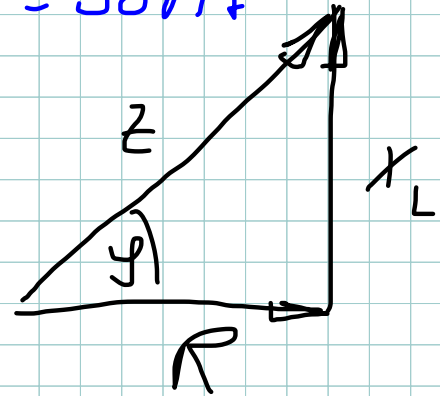

$$\cos \varphi = \frac{R}{Z}$$

$$Z = \frac{R}{\cos \varphi} = \frac{32}{0,12} = 266,6 \, \Omega$$

$$X_L = \sqrt{Z^2 - R^2} = \sqrt{266,6^2 - 32^2} = 264,7 \, \Omega$$

$$18.12 \quad R = 120 \Omega \quad L = 0,5 \text{ H}$$

$$f = 50 \text{ Hz} \quad U = 4 \text{ V}$$

$$X_L = 2\pi fL = 2 \cdot \pi \cdot 50 \cdot 0,5 = 157 \Omega$$

$$Z = \sqrt{R^2 + X_L^2} = \sqrt{120^2 + 157^2} = 197,6 \Omega$$


$$\cos \varphi = \frac{R}{Z} = \frac{120}{197,6} = 0,607$$

$$\varphi = \arccos(0,607) = 52,6^\circ$$

$$18.13 \quad U = 230 \text{ V} \quad f = 50 \text{ Hz}$$

$$S = 400 \text{ VA} \quad \cos \varphi = 0,8$$

$$\cos \varphi = \frac{P}{S}$$

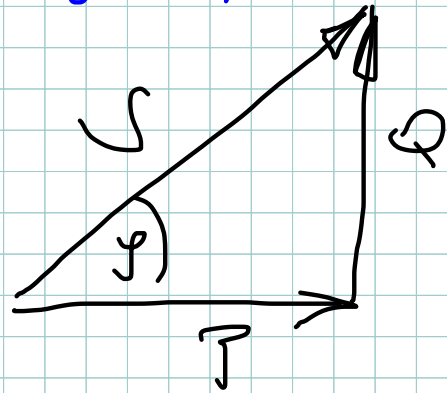

$$P = S \cdot \cos \varphi = 400 \cdot 0,8 = 320 \text{ W}$$

$$Q = \sqrt{S^2 - P^2} = \sqrt{400^2 - 320^2} = 240 \text{ VAR}$$

$$18.15 \quad U = 230 \text{ V} \quad f = 50 \text{ Hz}$$

$$I = 4,2 \text{ A} \quad P = 640 \text{ W}$$

$$S = U \cdot I = 230 \cdot 4,2 = 966 \text{ VA}$$

$$\cos \varphi = \frac{P}{S} = \frac{640}{966} = 0,66$$

$$Q = \sqrt{S^2 - P^2} = \sqrt{966^2 - 640^2} = 723,6 \text{ Var}$$

Markiert: $100 \text{ W} \hat{=} 1 \text{ cm}$